
 
 


Sinteza si implementarea circuitelor logice combinaționale

Multiplexoare

```
1 library IEEE;
2 use IEEE.std_logic_1164.all;
3 entity mux2_1 is
4 port (s: in std_logic;
5        D1,D0 : in std_logic;
6        Q : out std_logic);
7 end mux2_1;
8 architecture mux2_1_arch of mux2_1 is
9 begin
10    Q <= D1 when (s = '1') else D0;
11 end mux2_1_arch;
```

Mux 2 → 1


 



```

1 library IEEE;
2 use IEEE.std_logic_1164.all;
3 entity mux4in8b is
4 port(
5     s: in std_logic_vector (1 downto 0);
6     D3, D2, D1, D0: in std_logic_vector(1 to 8);
7     Q: out std_logic_vector(1 to 8)  );
8 end mux4in8b;
9 architecture mux4in8b_arch of mux4in8b is
10 begin
11     with S select Q <=
12         D0  when "00",
13         D1  when "01",
14         D2  when "10",
15         D3  when "11",
16         (others => 'U' ) when others; -- creaza un vector
17         -- de 8 biti din 'U', valoare
18         -- neinitializata
19 end mux4in8b_arch;


```

Mux 4 → 1 (8biti pe linie)

  

 

```
1  library IEEE;
2  use IEEE.std_logic_1164.all;
3  entity mux4in8b is
4  port(    S: in std_logic_vector (1 downto 0);
5          D3, D2, D1, DO: in std_logic_vector(1 to 8);
6          Q: out std_logic_vector(1 to 8)  );
7  end mux4in8b;
8  architecture mux4in8b_arch of mux4in8b is
9  begin
10  process (S, D3, D2, D1, DO)
11    begin
12    case S is
13      when "00" => Q <= DO;
14      when "01" => Q <= D1;
15      when "10" => Q <= D2;
16      when "11" => Q <= D3;
17      when others => Q <= (others =>'U') ;
18    end case;
19  end process;
20  end mux4in8b_arch;
21
```

 


Decodificatoare


```


1 library IEEE;
2 use IEEE.std_logic_1164.all;
3 entity dec3to8 is
4 port ( S: in std_logic_vector (2 downto 0); --intrari de selectare
5        EN: in std_logic; -- enable
6        Y: out std_logic_vector (7 downto 0)); -- iesirile sunt active pe zero
7 end dec3to8;
8 architecture dec3to8_arch of dec3to8 is
9 begin
10 process (S,EN)
11 begin
12   y <= "11111111";
13   if (en = '1') then
14     case S is
15     when "000" => Y(0) <= '0';
16     when "001" => Y(1) <= '0';
17     when "010" => Y(2) <= '0';
18     when "011" => Y(3) <= '0';
19     when "100" => Y(4) <= '0';
20     when "101" => Y(5) <= '0';
21     when "110" => Y(6) <= '0';
22     when "111" => Y(7) <= '0';
23     when others => null;

```

 


DC 3 → 8

 


 

```
1  library IEEE;
2    use IEEE.std_logic_1164.all;
3  USE ieee.numeric_std.ALL;
4  entity dec3to8 is
5    port ( S: in std_logic_vector (2 downto 0); --intrari de selectare
6          EN: in std_logic; -- enable
7          Y: out std_logic_vector (7 downto 0)); -- iesirile sunt active pe zero
8  end dec3to8;
9  architecture dec3to8_comp  of  dec3to8  is
10 begin
11   process (S,EN)
12     variable i : INTEGER range 0  to 7;
13     begin
14       Y <= "11111111";
15       if (EN = '1') then
16         for i  in  0  to  7  loop
17           if  i = to_integer(unsigned(S))  then  Y(i)  <=  '0' ;
18           end if;
19         end loop;
20       end if;
21     end process;
22  end dec3to8_comp ;
23
```

 



```
1      library IEEE;
2      use IEEE.std_logic_1164.all;
3  entity dec3to8_alt  is
4    port (S:  in std_logic_vector(2 downto 0);
5          En:  in std_logic;
6          Y_L:  out std_logic_vector(0 to 7));
7  end dec3to8_alt;
8  architecture dec3to8_alt  of dec3to8_alt  is
9  signal YI : STD_LOGIC_VECTOR (0 to 7);
10 begin
11     with S select YI  <=
12     "01111111"  when  "000" ,
13     "10111111"  when  "001" ,
14     "11011111"  when  "010" ,
15     "11101111"  when  "011" ,
16     "11110111"  when  "100" ,
17     "11111011"  when  "101" ,
18     "11111101"  when  "110" ,
19     "11111110"  when  "111" ,
20     "11111111"  when  others;
21     Y_L  <=  YI  when En ='1'   else "11111111";
22 end dec3to8_alt;
```

 

```


library IEEE;
use IEEE.std_logic_1164.all;
USE ieee.numeric_std.ALL;
entity dec3to8 is
port ( S: in std_logic_vector (2 downto 0); --intrari de selectare
        EN: in std_logic; -- enable
        Y: out std_logic_vector (7 downto 0)); -- iesirile sunt active pe zero
end dec3to8;
architecture dec3to8_comp of dec3to8 is
begin
process (S,EN)
variable i :INTEGER;
begin
Y <= "11111111";
if (EN = '1') then
i := to_integer(unsigned(S));
Y(i) <= '0';
end if;
end process;
end dec3to8_comp ;

```

  

Codificatoare în VHDL


 
Un codificator binar cu 2^n intrări și n ieșiri va genera la ieșire un cuvânt de cod la ieșire când se va activa o linie la intrare.



Programul VHDL al codificatorului $8 \rightarrow 3$ fără prioritate este descris comportamental, utilizând instrucțiunea process:



```
library ieee;
use ieee.std_logic_1164.all;
use ieee.std_logic_arith.all;
use ieee.std_logic_unsigned.all;
entity CD is
    port (en: in std_logic;
          X: in std_logic_vector (7 downto 0);
          Y: out std_logic_vector (2 downto 0));
end CD;
```

```
architecture CD_arch of CD is
begin
process (en, X)
begin
if (en='1') then Y<="ZZZ";
else
case (X) is
when "00000001" => Y <="000";
when "00000010" => Y <="001";
when "00000100" => Y <="010";
when "00001000" => Y <="011";
when "00010000" => Y <="100";
when "00100000" => Y <="101";
when "01000000" => Y <="110";
when "10000000" => Y <="111";
when others => null;
end case;
end if;
end process;
end;
```

  

Programul VHDL al codificatorului 8→3
cu prioritate este descris utilizând fluxul de date


```
1  library IEEE;
2    use IEEE.std_logic_1164.all;
3  entity CD is port (
4    X : in std_logic_vector (7 downto 0);
5    Y : out std_logic_vector (2 downto 0));
6  end CD;
7  architecture CD_arch of CD is
8  begin
9    Y <=
10      "000" when X(0)='1' else
11      "001" when X(1)='1' else
12      "010" when X(2)='1' else
13      "011" when X(3)='1' else
14      "100" when X(4)='1' else
15      "101" when X(5)='1' else
16      "110" when X(6)='1' else
17      "111" when X(7)='1' else|
18      "000";
19  end CD_arch;
20
```

  

```

1 library IEEE;
2 use IEEE.std_logic_1164.all;
3 entity CD_PR is port (
4     X : in std_logic_vector (7 downto 0);
5     Y : out std_logic_vector (2 downto 0));
6 end CD_PR;
7 architecture CD_PR_arch of CD_PR is
8 begin
9 process (X)
10 begin
11     Y <= "000";
12     if X(7)='1' then Y <= "111";
13     elsif X(6)='1' then Y <= "110";
14     elsif X(5)='1' then Y <= "101";
15     elsif X(4)='1' then Y <= "100";
16     elsif X(3)='1' then Y <= "011";
17     elsif X(2)='1' then Y <= "010";
18     elsif X(1)='1' then Y <= "001";
19     elsif X(0)='1' then Y <= "000";
20     end if;
21 end process;
22 end CD_PR_arch;
23

```

 

Sumatoare binare

Sumator cu transport succesiv pe 8 biți.


$$S = a \oplus b \oplus c_{in}$$

Expresiile logice pentru un sumator complet de 1 bit:


$$C_{out} = a \cdot b + c_{in} \cdot (a + b)$$

```
library IEEE;
use IEEE.std_logic_1164.all;
entity adder8 is port (
    a,b: in std_logic_vector (7 downto 0); -- semnalele de intrare
    cin: in std_logic; -- transport la intrare
    sum: out std_logic_vector(8 downto 0); -- semnale de ieșire
    cout: out std_logic); -- transport la ieșire
end adder8;
```

 
```
architecture adder8_arch of adder8 is
signal c: std_logic_vector(8 downto 0);
begin
process (a,b,cin,c)
begin
    c(0) <= cin;
    for i in 0 to 7 loop
        sum(i) <= a(i) xor b(i) xor c(i);
        c(i+1) <= (a(i) and b(i)) or (c(i) and (a(i) or b(i)));
    end loop;
    cout <= c(8);
end process;
end adder8_arch;
```



```
1  library ieee;
2  use ieee.std_logic_1164.all;
3  entity add_succ is
4      generic (n: natural := 4);
5      port (a, b: in std_logic_vector (n-1 downto 0);
6             cin: in std_logic;
7             s: out std_logic_vector (n-1 downto 0);
8             cout: out std_logic);
9  end add_succ;
10 architecture structural of add_succ is
11     signal c: std_logic_vector (n downto 0);
12 begin
13     c(0) <= cin;
14     gen: for i in 0 to n-1 generate
15         s(i) <= a(i) xor b(i) xor c(i);
16         c(i+1) <= (a(i) and b(i)) or (a(i) and c(i)) or
17                           (b(i) and c(i));
18     end generate;
19     cout <= c(n);
20 end structural;
21
22
```

 

```
1  library IEEE;
2  use IEEE.std_logic_1164.all;
3  use IEEE.std_logic_arith.all;
4
5  entity adder  is port (
6      a,b: in unsigned (7 downto 0);
7      c: in signed (7 downto 0);
8      d: in std_logic_vector (7 downto 0);
9      s: out unsigned (8 downto 0);
10     t: out signed (8 downto 0);
11     u: out signed (7 downto 0);
12     v: out std_logic_vector(8 downto 0)  );
13 end adder8;
14 architecture adder_arch of adder8 is
15 begin
16     s <= ('0' & a) + ('0' & b);
17     t <= a+c ;
18     u <= c + signed (d) ;
19     v <= c - unsigned (d) ;
20 end adder_arch;
21
22
```

 

```
s <= ('0' & a) + ('0' & b);
t <= a+c ;
u <= c + signed (d) ;
v <= c - unsigned (d) ;
```

	0		a	U	3	5	7	
	9		b	U	6	1	9	
	18		c	S	2	-5	-6	
	27		d	U	1	2	3	
	36		s	U	9	6	16	
	46		t	S	5	0	1	
	56		u	S	3	-3	-3	
	65		v	U	-	505	503	

