

Coduri sintetizabile

Constructii sintetizabile

ENTITY

- ARCHITECTURE
- CONFIGURATION
- PACKAGE
- Concurrent signal assignments
- PROCESS
- SIGNAL
- VARIABLE (non-shared)
- CONSTANT
- IF-ELSE
- CASE
- Loops (fixed iteration)
- Multi-dimensional arrays
- PORT
- GENERIC (constant)
- COMPONENT

Component & direct instantiation

- GENERATE
- FUNCTION
- PROCEDURE
- ASSERT (constant false)
- WAIT (one per process)
- TYPE
- SUBTYPE

Constructii nesintetizabile

- ACCESS
- ASSERT
- DISCONNECT
- FILE
- GROUP
- NEW
- Physical delay types
- PROTECTED
- SHARED VARIABLE
- Signal assignment delays

- Incomplete sensitivity list in combinatorial PROCESS blocks may result in differences between RTL & gate-level simulations
 - Synthesis tool synthesizes as if sensitivity list complete

```
PROCESS (a, b)  
y <= a AND b AND c;
```

**Incorrect Way – the simulated behavior is not
that of the synthesized 3-input AND gate**

```
PROCESS (a, b, c)  
y <= a AND b AND c;
```

Correct way for the intended AND logic !

- IF-ELSE (like WHEN-ELSE concurrent assignment) structure implies prioritization & dependency
 - Nth clause implies all N-1 previous clauses not true
 - Beware of needlessly “ballooning” logic

Logical Equation

$$(<\text{cond1}> \cdot A) + (<\text{cond1}>' \cdot <\text{cond2}> \cdot B) + (<\text{cond1}>' \cdot <\text{cond2}>' \cdot \text{cond3} \cdot C) + \dots$$

- Consider restructuring IF statements
 - May flatten the multiplexer and reduce logic

IF $<\text{cond1}>$ THEN
 IF $<\text{cond2}>$ THEN




IF $<\text{cond1}>$ AND $<\text{cond2}>$ THEN

- If sequential statements are mutually exclusive, individual IF structures may be more efficient

- Combinatorial processes that do not cover all possible input conditions generate latches

 
```
PROCESS (sel, a, b, c)
BEGIN
    IF sel = "001" THEN
        output <= a;
    ELSIF sel = "010" THEN
        output <= b;
    ELSIF sel = "100" THEN
        output <= c;
    END IF;
END PROCESS;
```



- Close all IF-ELSE structures


- If possible, assign "don't care's" to else clause for improved logic optimization
 
```
PROCESS (sel, a, b, c)
BEGIN
    IF sel = "001" THEN
        output <= a;
    ELSIF sel = "010" THEN
        output <= b;
    ELSIF sel = "100" THEN
        output <= c;
    ELSE
        output <= (OTHERS => 'X');
    END IF;
END PROCESS;
```




- Beware of building unnecessary dependencies
 - e.g. Outputs x, y, z are mutually exclusive, IF-ELSIF causes all outputs to be dependant on all tests & creates latches
 
```
PROCESS (sel,a,b,c)
BEGIN
  IF sel = "010" THEN
    x <= a;
  ELSIF sel = "100" THEN
    y <= b;
  ELSIF sel = "001" THEN
    z <= c;
  ELSE
    x <= '0';
    y <= '0';
    z <= '0';
  END IF;
END PROCESS;
```



- Separate IF statements and close
 
```
PROCESS (sel, a, b, c)
BEGIN
    IF sel = "010" THEN
        x <= a;
    ELSE
        x <= '0';
    END IF;
    IF sel = "100" THEN
        y <= b;
    ELSE
        y <= '0';
    END IF;
    IF sel = "001" THEN
        z <= c;
    ELSE
        z <= '0';
    END IF;
END PROCESS;
```




```
PROCESS (sel, a, b, c)
BEGIN
    x <= '0';
    y <= '0';
    z <= '0';
    IF sel = "010" THEN
        x <= a;
    END IF;
    IF sel = "100" THEN
        y <= b;
    END IF;
    IF sel = "001" THEN
        z <= c;
    END IF;
END PROCESS;
```

- Conditions where output is undetermined

```

output: PROCESS (filter)
BEGIN
  CASE filter IS
    WHEN idle =>
      nxt <= '0';
      first <= '0';
    WHEN tap1 =>
      sel <= "00";
      first <= '1';
    WHEN tap2 =>
      sel <= "01";
      first <= '0';
    WHEN tap3 =>
      sel <= "10";
    WHEN tap4 =>
      sel <= "11";
      nxt <= '1';
  END CASE;
END PROCESS output;

```

 

- Undetermined output conditions implies memory
- Latch generated for **ALL 3 outputs**

- Conditions where output is determined

```

output: PROCESS(filter)
BEGIN
    first <= '0';
    nxt <= '0';
    sel <= "00";
    CASE filter IS
        WHEN idle =>
        WHEN tap1 =>
            first <= '1';
        WHEN tap2 =>
            sel <= "01";
        WHEN tap3 =>
            sel <= "10";
        WHEN tap4 =>
            sel <= "11";
            nxt <= '1';
    END CASE;
END PROCESS output;

```

Signals Initialized

To remove latches & ensure outputs are never undetermined


- Use signal initialization at beginning of case statement (case statement only deals with changes)
- Use don't cares ('-') for WHEN OTHERS clause, if design allows (for better logic optimization)
- Manually set output in each case

UNINITIALIZED

```
ARCHITECTURE logic OF cmb_vari IS
BEGIN
    PROCESS(i0, i1, a)
        VARIABLE val :
            INTEGER RANGE 0 TO 1;
    BEGIN
        IF (a = '0') THEN
            val := val;
        ELSE
            val := val + 1;
        END IF;

        CASE val IS
            WHEN 0 =>
                q <= i0;
            WHEN OTHERS =>
                q <= i1;
        END CASE;
    END PROCESS;
END ARCHITECTURE logic;
```

Variable used without initialization

 


variable


```
ARCHITECTURE logic OF cmb_vari IS
BEGIN
    PROCESS(i0, i1, a)
        VARIABLE val :
            INTEGER RANGE 0 TO 1;
    BEGIN
        val := 0; ←
        IF (a = '0') THEN
            val := val;
        ELSE
            val := val + 1;
        END IF;

        CASE val IS
            WHEN 0 =>
                q <= i0;
            WHEN OTHERS =>
                q <= i1;
        END CASE;
    END PROCESS;
END ARCHITECTURE logic;
```

 *Assign initial value or
signal to variable*



 - Common cause of instability
- Behavior of loop depends on the relative propagation delays through logic
 - Propagation delays can change
- Simulation tools may not match hardware behavior




```

PROCESS (clk, clrn)
BEGIN
  IF clrn = '0' THEN
    q <= 0;
  ELSIF rising_edge (clk) THEN
    → q <= d;
  END IF;
END PROCESS;

clrn <= (ctrl1 XOR ctrl2) AND q;
  
```

 - All feedback loops should include registers



```

PROCESS (clk, clrn)
BEGIN
  IF clrn = '0' THEN
    q <= 0;
  ELSIF rising_edge (clk)
    q <= d;
  END IF;
END PROCESS;
  
```


```

PROCESS (clk)
BEGIN
  IF rising_edge (clk) THEN
    clrn <= (ctrl1 XOR ctrl2) AND q;
  END IF;
END PROCESS;
  
```

- Use parenthesis to define logic groupings
 - Increases performance
 - May increase utilization
 - Balances delay from all inputs to output
 - Circuit functionality unchanged


Unbalanced

$$z \leq a * b * c * d$$

 

Balanced

$$z \leq (a * b) * (c * d)$$

 


```

process(rst, clk)
variable tmp_q : std_logic_vector(7 DOWNTO 0);
begin
    if rst = '0' then
        tmp_q := (OTHERS => '0');
    elsif rising_edge(clk) then
        if updn = '1' then
            tmp_q := tmp_q + 1;
        else
            tmp_q := tmp_q - 1;
        end if;
    end if;
    q <= tmp_q;
end process;

```

 - Up/down counter
- 2 adders are mutually exclusive & can be shared (typically IF-THEN-ELSE with same operator in both choices)




```


process(rst, clk)
variable tmp_q : std_logic_vector(7 DOWNTO 0);
variable dir : integer range -1 to 1;
begin
    if rst = '0' then
        tmp_q := (OTHERS => '0');
    elsif rising_edge(clk) then
        if updn = '1' then
            dir := 1;
        else
            dir := -1;
        end if;
        tmp_q := tmp_q + dir;
    end if;
    q <= tmp_q;
end process;

```

 - Up/down counter
- Only one adder required



 
$$y \leq a * b * c$$
$$z \leq b * c * d$$



4 Multipliers!

$$y \leq a * (b * c)$$

$$z \leq (b * c) * d$$

 

3 Multipliers!

- This is called sharing common subexpressions
- Some synthesis tools do this automatically, but some don't!
- Parentheses guide synthesis tools
- If $(b*c)$ is used repeatedly, assign to temporary signal