 


1. Registru pe 8 biți cu încărcare paralelă și resetare asincronă

```

library ieee;
use ieee.std_logic_1164.all;
entity registru1 is
port ( clk, reset, ld: in std_logic;
       din: in std_logic_vector(7 downto 0);
       dout: out std_logic_vector(7 downto 0));
end registru1;
architecture behavior of registru1 is
signal n_state: std_logic_vector(7 downto 0);
signal p_state : std_logic_vector(7 downto 0);
begin
begin
process(clk, reset)
begin
if (reset = '0') then p_state <= (others => '0'); --resetare asincrona
elsif (clk'event and clk = '1') then
  if (ld='1') then n_state <= din; --încarcare paralela
    else null;
  end if;
  p_state <= n_state;
end if;
end process;
dout <= p_state;
end behavior;

```





## 2. Registrul bidirectional cu incarcare seriala

```

library ieee;
use ieee.std_logic_1164.all;
use ieee.std_logic_arith.all;
use ieee.std_logic_unsigned.all;
entity registru2 is
    port (clk, si, left_right: in std_logic;
          Po: out std_logic_vector (7 downto 0));
end registru2;
architecture beh of registru2 is
signal tmp: std_logic_vector (7 downto 0);
begin
    begin
        process (clk)
        begin
            if (clk'event and clk='1') then
                if (left_right='0') then
                    tmp<=tmp(6 downto 0) & si; --deplasare stanga si incarcare seriala
                else
                    tmp<=si & tmp(7 downto 1); --deplasare dreapta si incarcare seriala
                end if;
            end if;
        end process;
        po<=tmp; --iesire paralela
    end beh;

```

  


### 3.Registrul deplasare stanga cu incarcare paralela, activ pe frontul pozitiv al semnalului de ceas

```

library ieee;
use ieee.std_logic_1164.all;
use ieee.std_logic_arith.all;
use ieee.std_logic_unsigned.all;
entity registru3 is
    port (clk, LD, SI : in std_logic;
          D: in std_logic_vector (7 downto 0);
          Po: out std_logic_vector (7 downto 0));
end registru3;
architecture beh of registru3 is
signal tmp: std_logic_vector (7 downto 0);
begin
    begin
        process (CLK, LD, D)
        begin
            if (LD='1') then
                tmp <= D; --încarcare paralela
            elsif (CLK'event and CLK='1') then
                tmp <= tmp(6 downto 0) & SI;
            end if;
        end process;
        Po<=tmp; --iesire paralela
    end beh;

```

 

Proiectați un registru de deplasare pe 3 biți, activ pe frontul negativ al semnalului de ceas, cu resetare sincronă, încărcare paralelă, care efectuează operația de împărțire la 2.