 


1. Numărător direct de 8 biți cu semnale asincrone de resetare și setare.

```

library ieee;
use ieee.std_logic_1164.all;
use ieee.std_logic_unsigned.all;
entity num1 is
    port (clk: in std_logic;
          rst, set: in std_logic;
          en, load: in std_logic;
          data: in std_logic_vector (7 downto 0);
          num: out std_logic_vector (7 downto 0));
end num1;
architecture arh_num1 of num1 is
    signal tmp: std_logic_vector (7 downto 0);
    begin
        cnt: process (rst, set, clk)
            begin
                if (rst = '1') then
                    tmp <= (others => '0');
                elsif (set = '1') then
                    tmp <= (others => '1');
                elsif (clk'event and clk = '1') then
                    if (load = '1') then
                        tmp <= data;
                    elsif (en = '1') then
                        tmp <= tmp + 1;
                    end if;
                end if;
            end process cnt;
            num <= tmp;
    end arh_num1;

```





2. Numărător pe 4 biți reversibil cu încărcare sincronă

```

library ieee;
use ieee.std_logic_1164.all;
use ieee.std_logic_unsigned.all;
entity num2 is
port (clk, clr, load, up, down: in std_logic;
      data: in std_logic_vector(3 downto 0);
      count: out std_logic_vector(3 downto 0));
end num2;
architecture count4 of num2 is
signal cnt: std_logic_vector(3 downto 0);
begin
  process (clr, clk)
  begin
    if clr='1' then cnt<="0000";
    elsif (clk'event and clk='1') then
      if load='1' then cnt<=data;
      elsif up='1' then
        if cnt="1111" then cnt <="0000";
        else cnt<=cnt+1;
        end if;
      elsif down='1' then
        if cnt="0000" then cnt<="1111";
        else cnt<=cnt-1;
        end if;
      else
        cnt<=cnt;
      end if;
    end if;
  end process;
  count<=cnt;
end count4;

```

 


 


3. Numarator reversibil cu modul arbitrar.

```

library ieee;
use ieee.std_logic_1164.all;
use ieee.std_logic_unsigned.all;
entity num3 is
port (clk, clr, load, up, down: in std_logic;
      data: in std_logic_vector(3 downto 0);
      count: out std_logic_vector(3 downto 0));
end num3;
architecture count4 of num3 is
signal cnt: std_logic_vector(3 downto 0);
begin
    process (clr, clk)
    begin
        if clr='1' then cnt<="0000";
        elsif (clk'event and clk='1') then
            if load='1' then cnt<=data;
            elsif up='1' then
                if cnt="1100" then cnt <="0000";
                else cnt<=cnt+1;
                end if;
            elsif down='1' then
                if cnt="0000" then cnt<="1100";
                else cnt<=cnt-1;
                end if;
            else
                cnt<=cnt;
            end if;
        end if;
        count<=cnt;
    end process;
end count4;

```

  

Proiectați un numărător cu **semnal asincron de resetare**, **încărcare paralelă**, activ pe **frontul negativ** al semnalului de ceas, care numara din **2 in 2** . Starea initiala **4**. Starea finala **14**.